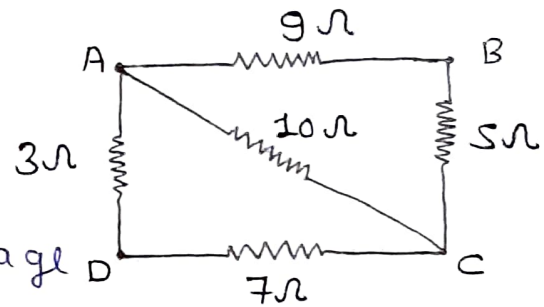


Assignment - 1 (Current Electricity)

Subject - Physics

Q1-1: In a discharge tube, the number of hydrogen ions drifting across a section per second is 1.0×10^{18} , while the no. of electrons drifting in the opposite direction across another cross-section is 2.7×10^{18} per second. If the supply voltage is 230V, what is the effective resistance of the tube?

Q1-2: Find equivalent resistance between the points A and C.




Q1-3: If a copper wire is stretched to make it 0.1% longer, what is the percentage change in its resistance?

Q1-4: A and B are two points on a circular ring made of uniform wire of resistance R. If the part AB of ring subtends an angle θ at the centre C of the ring as shown in figure. Find the resistance of the ring between the points A and B.




Q1-5: Find equivalent Resistance of network between

- (a) A and B
- (b) A and C

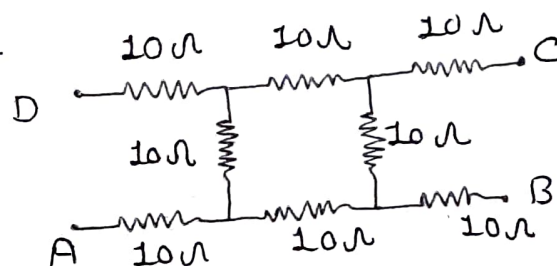


Q1-6: find equivalent Resistance of network shown in figure between points A and B when

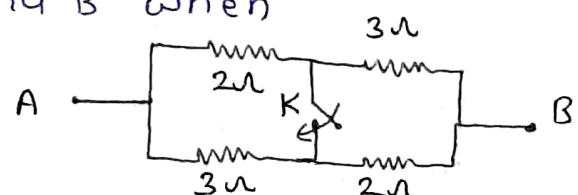
- (a) the Key K is open
- (b) the Key K is closed.



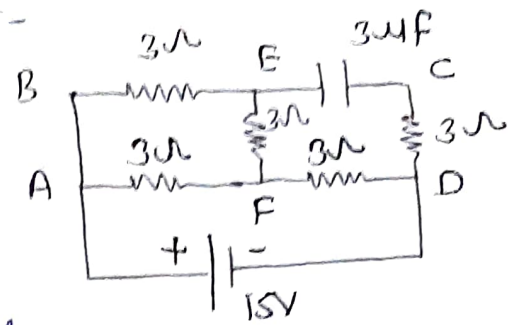Q1-7: In circuit shown in figure determine the potential difference across the capacitor-




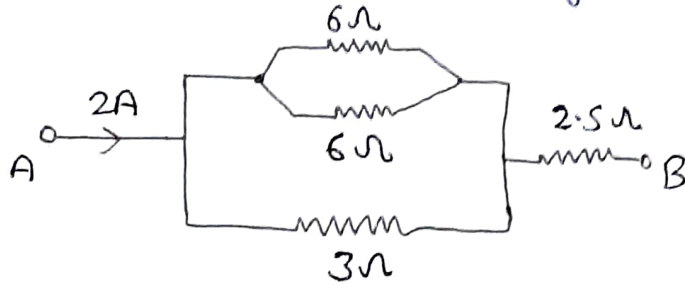Q1-8: find potential difference between the points A and B for the network shown in figure-



Q1-9: A standard coil marked 2Ω is found to have a resistance of 2.118Ω at 30°C . Calculate the temperature at which the marking is correct. The temp. coefficient of resistance of the material of the coil is $0.0042/^\circ\text{C}$.

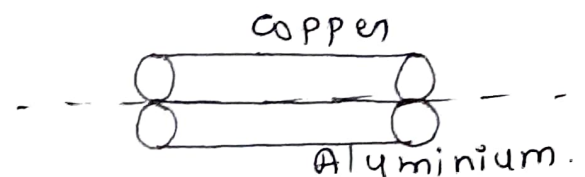Q1-10: A copper rod of length 20cm and cross-sectional area 2mm^2 is joined with a similar aluminium rod as shown in figure. Find resistance of the combination between the ends. $\rho_{\text{Cu}} = 1.7 \times 10^{-8}\Omega\text{-m}$ and $\rho_{\text{Al}} = 2.6 \times 10^{-8}\Omega\text{-m}$



Pratyanshu Porwal

Pratyanshu Porwal