

G.N. National Public School Garakhpur


Assignment-1 (Physics)

Topic- Capacitor


Q1-1: 27 drops of same size are charged at 220V each. They combine to form a bigger drop. Calculate the potential of bigger drop.

Q1-2: The effective capacitance of two capacitors are $3\mu F$ and $16\mu F$, when they are connected in series and parallel respectively. Compute the capacitance of each capacitor.

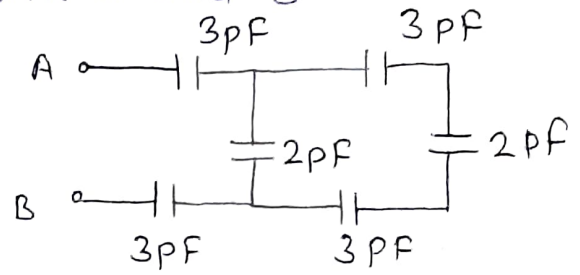Q1-3: Calculate equivalent capacitance of the network shown in figure between point A and B -




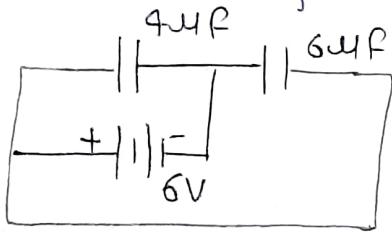Q1-4: Two capacitors C_1 and C_2 are connected to a battery of 6V as shown in figure find charge on each capacitor.



Q1-5: A capacitor of $4\mu F$ is connected to 400V supply. It is then disconnected and connected to an uncharged capacitor of $2\mu F$. Calculate the common potential after the capacitors are connected together.

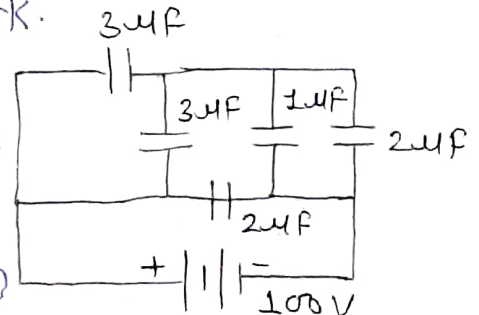Q1-6: figure shows a network of five capacitors are connected to a 100V supply. Calculate the total charge and energy stored in the network.




Q1-7: Find ratio of the potential differences that must be applied across
(i) parallel (ii) series combination of two identical capacitors so that the energy stored in two cases becomes same?

Q!-8: Keeping the voltage of the charging source constant what would be the percentage change in the energy stored in a parallel plate capacitor, if the separation between its plates were to be decreased by 10%?

Q!-9: A capacitor is made of a flat plate of Area A and a second plate having a stair-like structure as shown in figure-


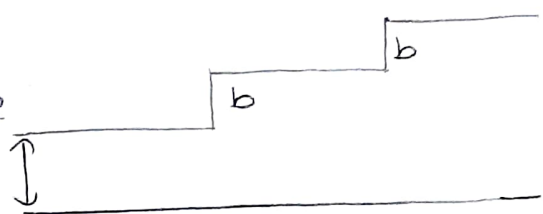
The height of first step is d while those of subsequent steps is d b as shown in figure calculate the capacitance of the structure.




Q!-10: Two capacitors of $25\mu F$ and $100\mu F$ are connected in series to a source of $120V$. Keeping their charges unchanged they are separated and connected in parallel to each other find out-

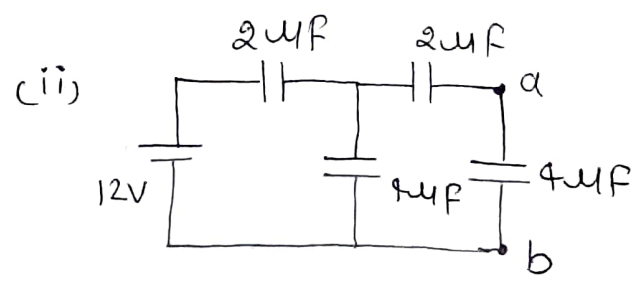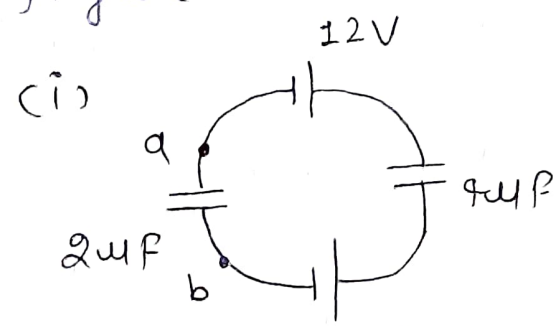- (a) Potential diff between the plates of each capacitor
- (b) Energy loss in the process.

Q!-11: Find potential difference $V_a - V_b$ between the points a and b as shown in each part of the figure-



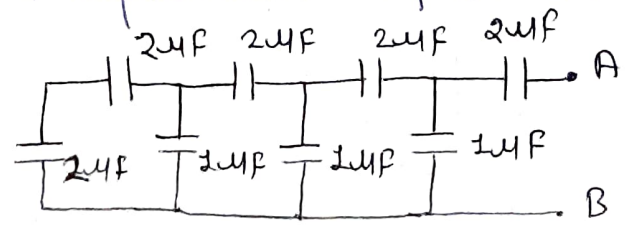Q!-12: Find equivalent capacitance between A and B -



Pratyanshu Porwal